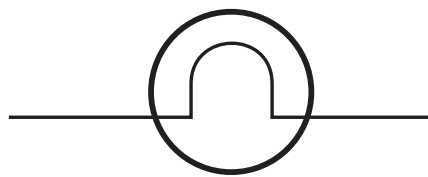
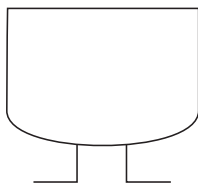
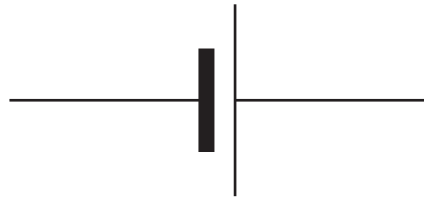
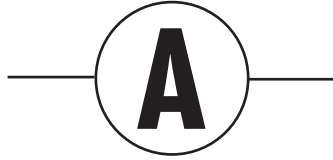


# Circuit symbols

Label the circuit symbols. Use the words at the bottom of the page to help you.



closed switch

battery

open switch

buzzer

bulb

ammeter

voltmeter